




CSE 140 Discussion #2

Karnaugh Maps & 2-level Logic Minimization

Chengmo Yang

04/13/2009



Concepts for sum-of-product forms

- **Literal:** a variable or its compliment
- **Minterm:** a product involving all the inputs to the function with each variable appearing exactly ones
- **Implicant:** product (AND) of one or more literals
- **Prime Implicant:** an implicant not contained in any other bigger implicant with fewer literals
- **Essential Prime Implicant:** a prime implicant containing a minterm which is not contained in any other prime implicant



Concepts for product-of-sum forms

- **Literal:** a variable or its compliment
- **Maxterm:** a sum involving all the inputs to the function with each variable appearing exactly once
- **Implicate:** sum (OR) of one or more literals
- **Prime Implicate:** an implicate not contained in any other bigger implicate with fewer literals
- **Essential Prime Implicate:** a prime implicate containing a maxterm which is not contained in any other prime implicate



Minterm vs. maxterm representation

$$\begin{aligned}F &= a \text{ xor } b \text{ xor } c \\&= (a'b+ab') \text{ xor } c \\&= (a'b+ab')c' + (a'b'+ab)c \\&= a'bc' + ab'c' + a'b'c + abc \\&= \Sigma (1, 2, 4, 7) \\&= \Pi (0, 3, 5, 6) \\&= (a+b+c)(a+b'+c')(a'+b+c')(a'+b'+c)\end{aligned}$$

$$\begin{aligned}F' &= \Sigma (0, 3, 5, 6) \\&= a'b'c' + a'bc + ab'c + abc' \\&= \Pi (1, 2, 4, 7) \\&= (a+b+c')(a+b'+c)(a'+b+c)(a'+b'+c)\end{aligned}$$

Questions:

$$F = a \text{ xor } b$$

$$G = a \text{ xnor } b$$

$$F = G \text{ or } F = G' ?$$

$$F = a \text{ xor } b \text{ xor } c$$

$$G = a \text{ xnor } b \text{ xnor } c$$

$$F = G \text{ or } F = G' ?$$

K-Map example

Exercises 2.1(d) in text book

a	b	c	d	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

F		cd		ab			
				00	01	11	10
00	00	1	1	1	1		
	01	0	0	0	0		
	11	0	0	0	1		
	10	1	0	0	1		

K-Map example

Exercises 2.1(d) in text book

a	b	c	d	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Each minterm \rightarrow 1-cell

Minterm $a'b'c'd$

F		cd			
		00	01	11	10
ab	00	1	1	1	1
	01	0	0	0	0
	11	0	0	0	1
	10	1	0	0	1

Implicant $ab'd'$
Prime?
Essential?


K-Map example

Exercises 2.1(d) in text book

a	b	c	d	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Each maxterm \rightarrow 0-cell

Maxterm
 $a'+b'+c+d'$

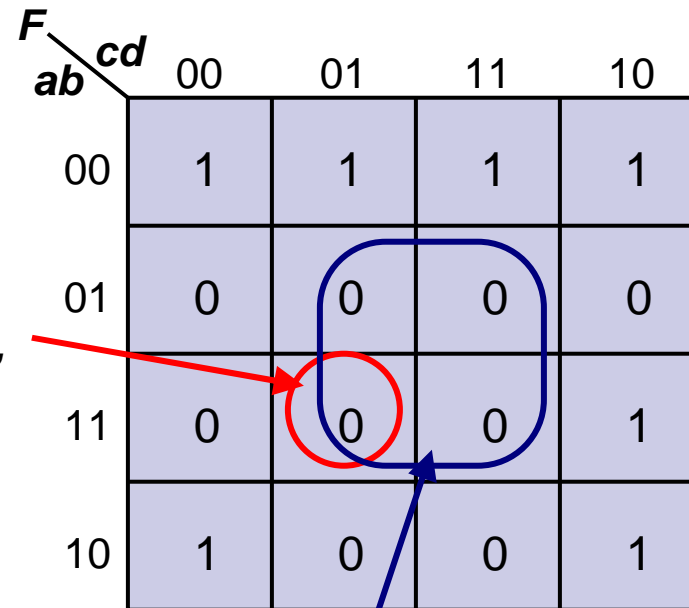

Implicate $b'+d'$
Prime?
Essential?




2-level logic minimization

Sum-of-product form:

- Find all prime implicants (PIs)
- Find all essential prime implicants (EPIs)
- Select all EPIs
- Select a minimum number of PIs that cover the remaining minterms

Product-of-sum form:

- Find implicates instead of implicants

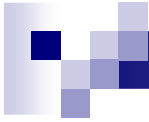

K-Map example for SoP


PIs: $a'b'$, $b'd'$, acd'

EPIs: $a'b'$, $b'd'$, acd'

$$F = a'b' + b'd' + acd'$$

a	b	c	d	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

F $ab \backslash cd$	00	01	11	10
00	1	1	1	1
01	0	0	0	0
11	0	0	0	1
10	1	0	0	1

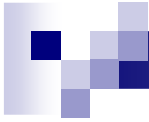

K-Map example for PoS

PIs: $a+b'$, $b'+c$, $b'+d'$, $a'+d'$ $F = (a+b')(b'+c)(a'+d')$
EPIs: $a+b'$, $b'+c$, $a'+d'$ $= (a'b+bc'+ad)'$

a	b	c	d	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

F		cd		ab			
				00	01	11	10
00	00	1	1	1	1		
	01	0	0	0	0		
	11	0	0	0	1		
	10	1	0	0	1		



2-level combinational circuit

- Sum-of-product form \rightarrow 2-level AND-OR gates
- Product-of-sum form \rightarrow 2-level OR-AND gates

$$F = a'b' + b'd' + acd'$$

Level1: two 2-AND, one 3-AND
Level2: one 3-OR

$$F = (a+b')(b'+c)(a'+d')$$

Level1: three 2-OR
Level2: one 3-AND


2-level combinational circuit

- Sum-of-product form \rightarrow 2-level AND-OR gates
- Product-of-sum form \rightarrow 2-level OR-AND gates

$$F = a'b' + b'd' + acd'$$

Level1: two 2-AND, one 3-AND


Level2: one 3-OR

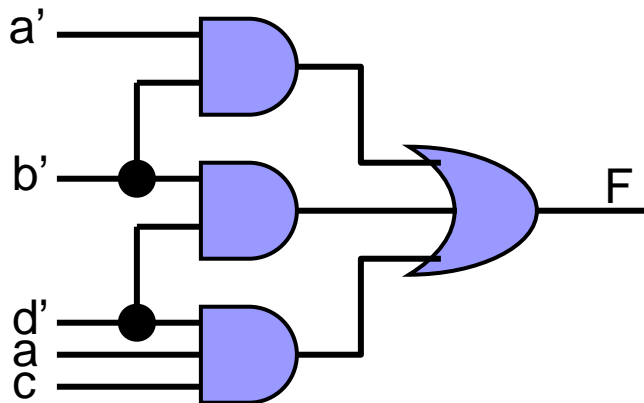

$$F = (a+b')(b'+c)(a'+d')$$

Level1: three 2-OR


Level2: one 3-AND

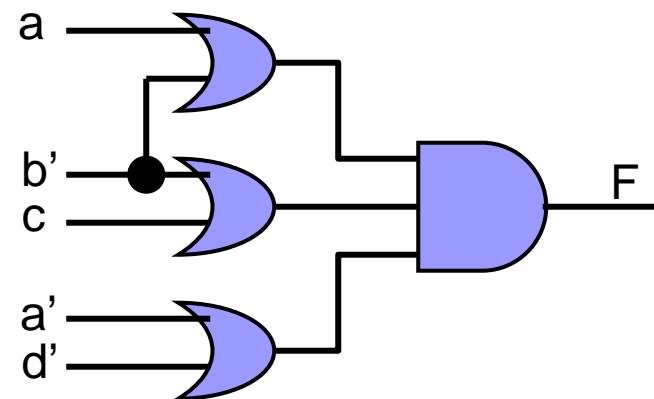


2-level logic transformation

- SoP form \rightarrow 2-level AND-OR gates \rightarrow 2-level NAND gates
- PoS form \rightarrow 2-level OR-AND gates \rightarrow 2-level NOR gates
- NAND and NOR: universal gates

$$F = a'b' + b'd' + acd'$$

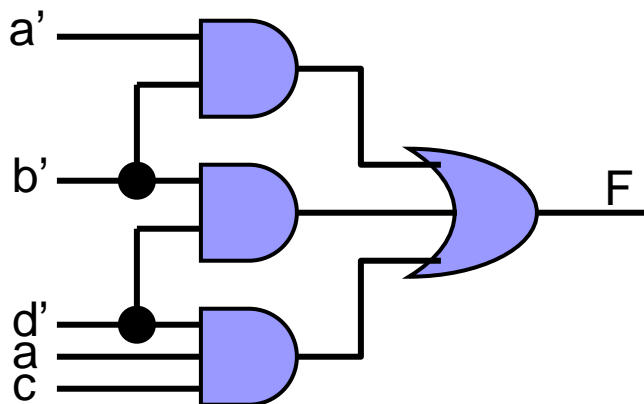


$$F = (a+b')(b'+c)(a'+d')$$

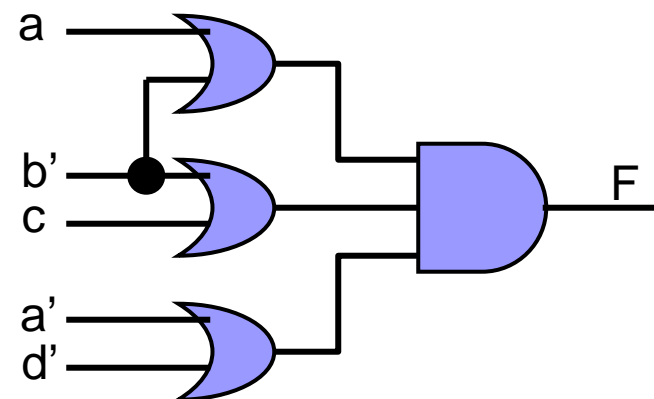


2-level logic transformation

- SoP form \rightarrow 2-level AND-OR gates \rightarrow 2-level NAND gates
- PoS form \rightarrow 2-level OR-AND gates \rightarrow 2-level NOR gates
- NAND and NOR: universal gates
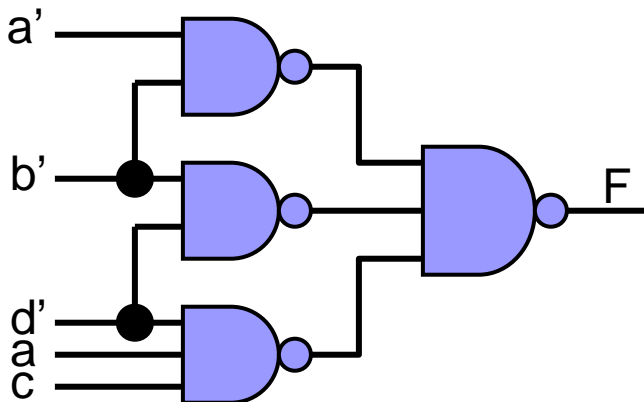
$$F = a'b' + b'd' + acd'$$
$$= ((a'b')' (b'd')' (acd')')'$$


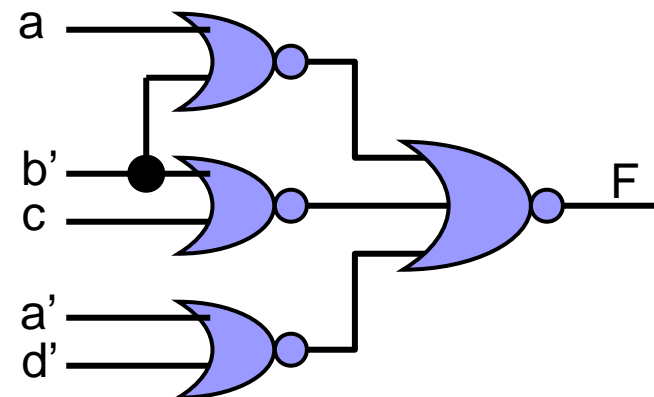
$$F = (a+b')(b'+c)(a'+d')$$
$$= ((a+b')' + (b'+c)' + (a'+d')')'$$



Another example

$$F = abc + abd + abe + acd + ace + (a+d+e)' + b'c'd + b'c'e + b'd'e' + c'd'e'$$

$$= abc + abd + abe + acd + ace + a'd'e' + b'c'd + b'c'e + b'd'e' + c'd'e'$$

Truth table for F when $a = 0$. The variables b, c, d, e are represented by the rows and columns of the table.

$bc \backslash de$	00	01	11	10
00	1	0	0	0
01	1	0	0	0
11	1	0	0	0
10	1	0	0	0

$a = 0$

Truth table for F when $a = 1$. The variables b, c, d, e are represented by the rows and columns of the table.

$bc \backslash de$	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	1	1	1	1
10	0	1	1	1

$a = 1$

Another example

$$F = abc + abd + abe + acd + ace + (a+d+e)' + b'c'd + b'c'e + b'd'e' + c'd'e'$$

$$= abc + abd + abe + acd + ace + a'd'e' + \underline{b'c'd + b'c'e + b'd'e' + c'd'e'}$$

F

<i>bc</i> \ <i>de</i>	00	01	11	10
00	1	1	1	1
01	1	0	0	0
11	1	0	0	0
10	1	0	0	0

$a = 0$

F


<i>bc</i> \ <i>de</i>	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$a = 1$


Another example

$$F = abc + abd + abe + acd + ace + (a+d+e)' + b'c'd + b'c'e + b'd'e' + c'd'e'$$
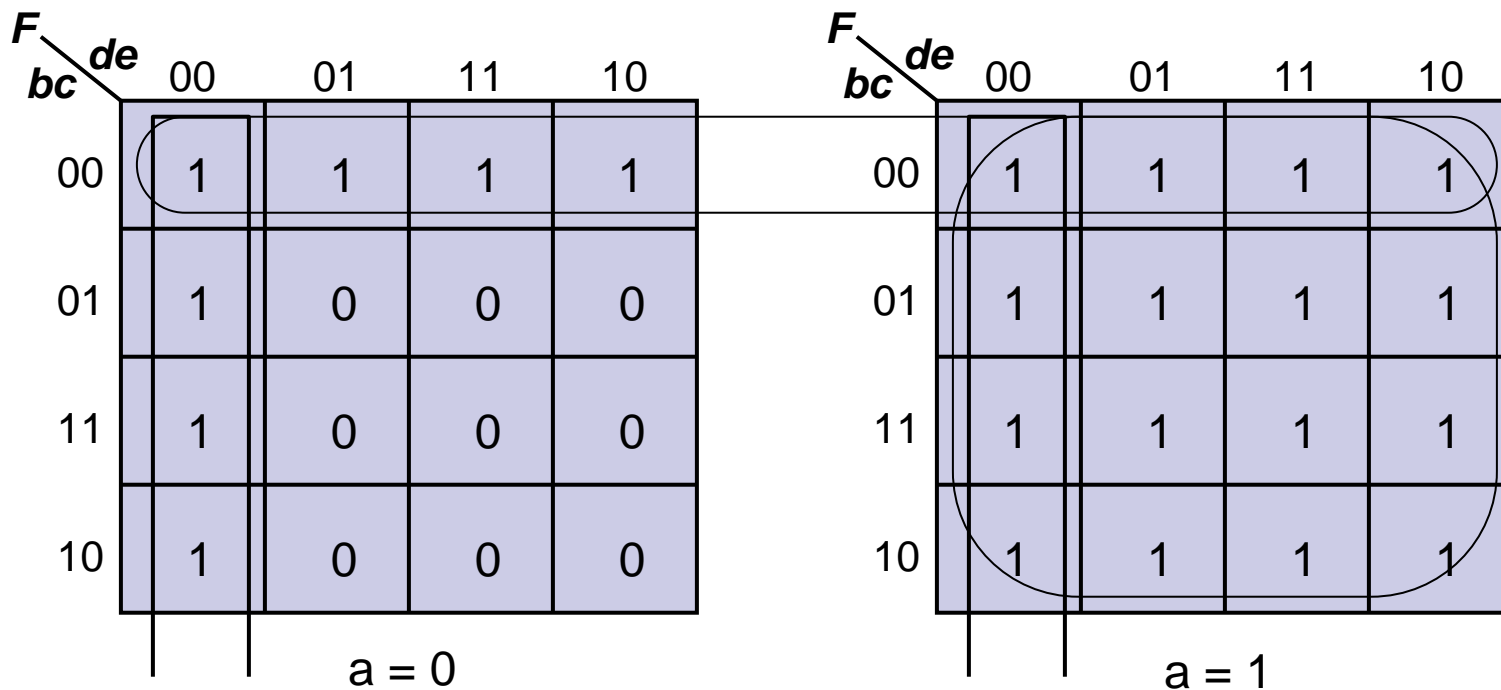
$$= abc + abd + abe + acd + ace + a'd'e' + b'c'd + b'c'e + b'd'e' + c'd'e'$$




$$F = a + d'e' + b'c'$$

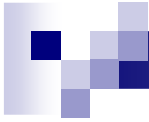

K-Map with don't cares

a	b	c	d	F	G
0	0	0	0	0	1
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	1	1
0	1	0	1	x	x
0	1	1	0	x	x
0	1	1	1	x	x
1	0	0	0	x	x
1	0	0	1	x	x
1	0	1	0	x	x
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	0

F		cd		ab			
				00	01	11	10
00	00	0	1	1	1		
	01	1	x	x	x		
	11	0	0	1	0		
	10	x	x	0	x		

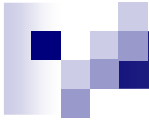


K-Map with don't cares

PIs: $a'b$, $a'c$, $a'd$, bcd

EPIs: $a'b$, $a'c$, $a'd$, bcd

$$F = a'b + a'c + a'd + bcd$$

a	b	c	d	F	G
0	0	0	0	0	1
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	1	1
0	1	0	1	x	x
0	1	1	0	x	x
0	1	1	1	x	x
1	0	0	0	x	x
1	0	0	1	x	x
1	0	1	0	x	x
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	0

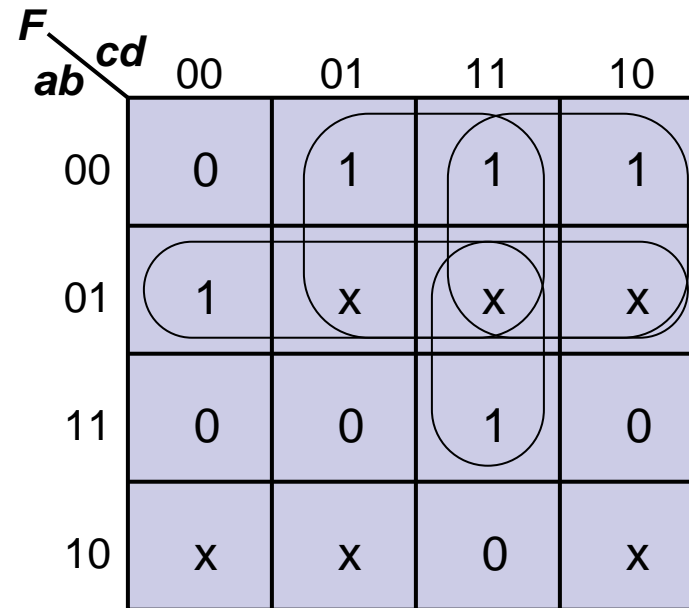

Question: minimum PoS for G?