

CSE 140 Discussion #3

Midterm 1 Review

Mingjing Chen
04/20/2009

Course materials covered so far

- **Boolean algebra**
 - Axioms & theorems
- **Basic gates**
- **Boolean function representations**
 - Canonical form, SoP, PoS
- **Two-level function minimization**
 - Kmap, Quine-McCluskey Approach
- **Other issues**
 - Shannon expansion

Boolean Algebra (1)

Prove $a'c' + ab + ac + a'b' = a'c' + ab + b'c$

Proof: $a'c' + ab + ac + a'b'$

$$= a'c' + ab + (ac + a'b') \quad \text{associativity}$$

$$= a'c' + ab + (ac + a'b' + b'c) \quad \text{consensus}$$

$$= a'c' + ab + ac + a'b' + b'c + b'c \quad \text{idempotency}$$

$$= (a'c' + b'c + a'b') + (ab + b'c + ac) \quad \text{commutativity+associativity}$$

$$= (a'c' + b'c) + (ab + b'c) \quad \text{consensus}$$

$$= a'c + ab + b'c \quad \text{idempotency}$$

Boolean Algebra (2)

$$(a + c)(a' + c')(b' + c + d')(a + b' + d') = (a + c)(a' + c')(b' + d')$$

Proof: $(a + c)(a' + c')(b' + c + d')(a + b' + d')$

$$= (a + c) (a' + c') ((ac) + (b' + d')) \quad \text{distributivity}$$

$$= (a + c) (a' + c') ac + (a + c) (a' + c') (b' + d') \quad \text{distributivity}$$

$$= (a + c) (a'ac + c'ac) + (a + c) (a' + c') (b' + d') \quad \text{distributivity}$$

$$= (a + c) (0 + 0) + (a + c) (a' + c') (b' + d') \quad \text{complement}$$


$$= 0 + (a + c) (a' + c') (b' + d') \quad \text{nullity}$$

$$= (a + c) (a' + c') (b' + d') \quad \text{identity}$$

Universal Gates (1)

Universality check: $\{f(x,y)\}$, where $f(x, y) = x+y'$, assuming 0 & 1 are available as inputs

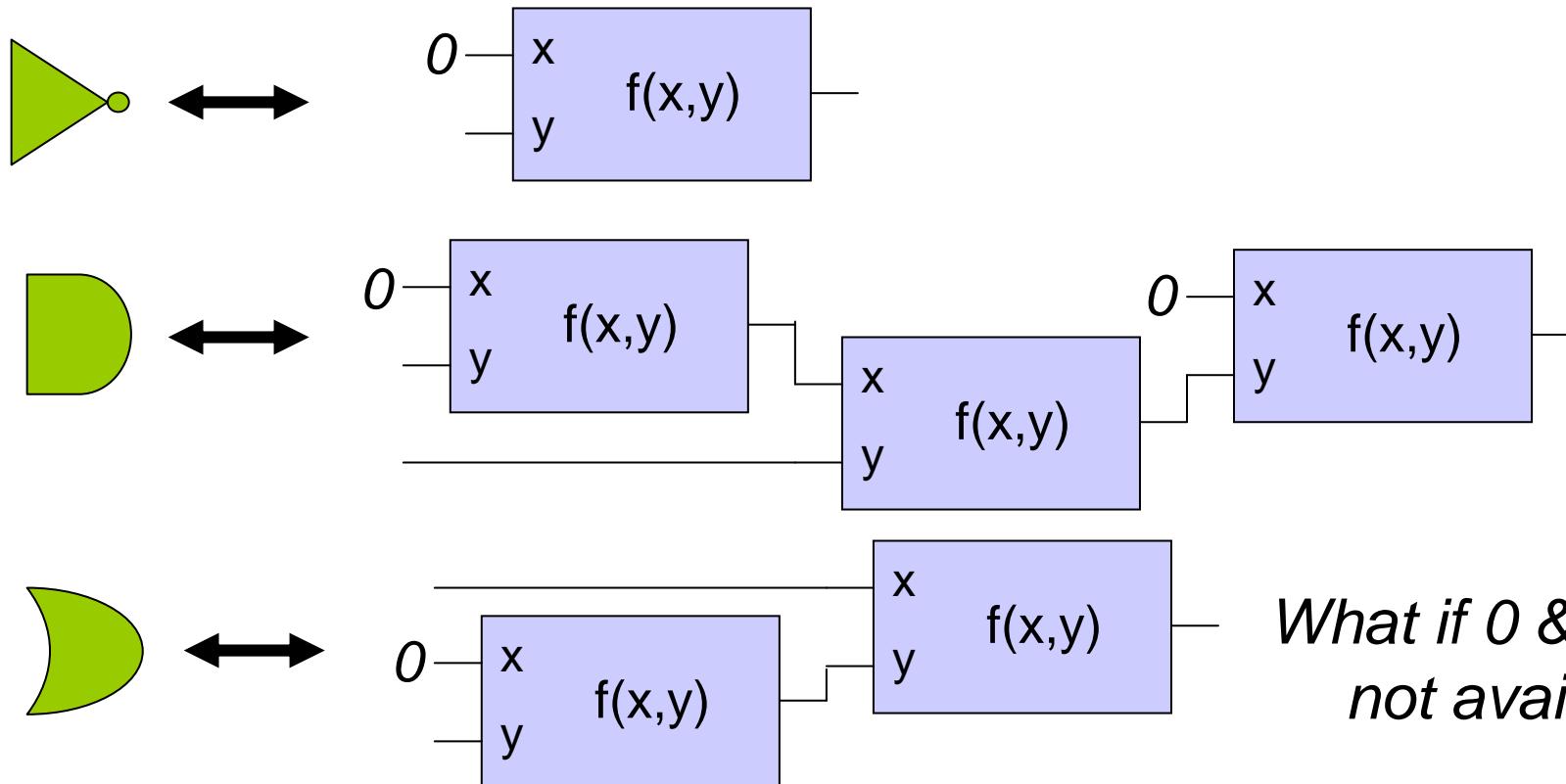
Strategy: Construct AND, OR & NOT using $\{f(x,y)\}$



Universal Gates (2)

Universality check: $\{f(x,y,z)\}$, where $f(x, y, z) = xz + y'z'$,
assuming 0 & 1 are available as inputs

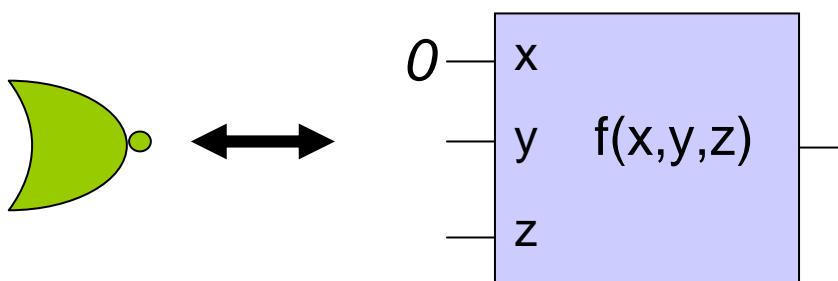Connect x to 0 $\rightarrow f(x,y,z) = y'z' = (y+z)'$ \rightarrow NOR gate
constructed



NOR gate universal $\rightarrow f(x,y,z)$ universal

Two-level Logic Minimization: SoP

	ab cd	00	01	11	10
00	0	1	x	1	
01	1	1	1	0	
11	0	0	1	0	
10	x	x	x	1	

Essential prime implicants:

$a'c'd$, ad' , ab

Non-essential prime implicants:

bc' , bd' , cd ,

Minimum SoP cover:

$a'c'd + ad' + ab + bc'$

$a'c'd + ad' + ab + bd'$

Essential prime implicants must be included in the cover!

Two-level Logic Minimization: PoS

ab \ cd	00	01	11	10
00	0	1	x	0
01	1	0	x	1
11	0	1	1	0
10	x	1	1	0

Essential prime implicants:
 $b+d$, $b+c'$, $b'+c+d'$

Non-essential prime implicants:
 $a'+c+d$

Minimum PoS cover:
 $(b+d)(b+c')(b'+c+d')$

Essential prime implicants must be included in the cover!

Shannon Expansion

$$f(x, y) = x f(1, y) + x' f(0, y) \quad \text{Why?}$$

If $x = 0$ $f(0, y) = 0 f(1, y) + 1 f(0, y)$

$$f(x, y) = x f(1, y) + x' f(0, y)$$

If $x = 1$ $f(1, y) = 1 f(1, y) + 0 f(0, y)$

Can be used to simplify some Boolean equations

Shannon Expansion Example

$$f(x, y) = x'y \oplus (x+y') \oplus y \oplus x \oplus (x'+y')$$

$$f(0, y) = y \oplus y' \oplus y \oplus 0 \oplus 1 = y$$

$$f(1, y) = 0 \oplus 1 \oplus y \oplus 1 \oplus y' = 1$$

$$\begin{aligned} f(x, y) &= x f(1, y) + x' f(0, y) = x + x'y \\ &= x + xy + x'y \\ &= x + y \end{aligned}$$