 


CSE 140 Discussion

Chengmo Yang

Mingjing Chen

06/01/09





Overflow

Prove that for two's complement number system arithmetic, the overflow of the addition is determined by the last two carry bits, i.e.

$$\text{overflow flag} = c_n \oplus c_{n-1}.$$

Overflow cases:

- Adding two positive numbers \rightarrow overflow iff $s_{n-1} = 1$

$$a_{n-1} = b_{n-1} = 0 \rightarrow c_n \text{ always } = 0, s_{n-1} = 1 \text{ iff } c_{n-1} = 1 \\ \rightarrow \text{overflow iff } c_n \oplus c_{n-1} = 1$$

- Adding two negative numbers \rightarrow overflow iff $s_{n-1} = 0$


$$a_{n-1} = b_{n-1} = 1 \rightarrow c_n \text{ always } = 1, s_{n-1} = 0 \text{ iff } c_{n-1} = 0 \\ \rightarrow \text{overflow iff } c_n \oplus c_{n-1} = 1$$

- Adding two numbers with different signs \rightarrow never overflow **Why?**

$$a_{n-1} \neq b_{n-1} \rightarrow c_n \text{ always } = c_{n-1} \rightarrow c_n \oplus c_{n-1} = 0$$

$$3 + 5 = 8 \\ \begin{array}{r} 0 & 1 & 1 & 1 \\ 0 & 0 & 1 & 1 \\ + & 0 & 1 & 0 & 1 \\ \hline 1 & 0 & 0 & 0 \end{array}$$
 
$$-4 + -5 = -9 \\ \begin{array}{r} 1 & 0 & 1 & 1 \\ 1 & 1 & 0 & 0 \\ + & 1 & 0 & 1 & 1 \\ \hline 0 & 1 & 1 & 1 \end{array}$$



Carry Look Ahead (CLA) Adder

A carry look ahead adder inputs two-bit numbers ($a_1; a_0$) and ($b_1; b_0$), and a carry in c_0 . Use a minimal two-level NAND gate network to implement the carry out c_2 .

$$c_1 = a_0b_0 + (a_0+b_0)c_0$$

$$\begin{aligned} c_2 &= a_1b_1 + (a_1+b_1)c_1 \\ &= a_1b_1 + (a_1+b_1)a_0b_0 + (a_1+b_1)(a_0+b_0)c_0 \\ &= a_1b_1 + a_1a_0b_0 + b_1a_0b_0 + a_1a_0c_0 + b_1a_0c_0 + a_1b_0c_0 + b_1b_0c_0 \end{aligned}$$

1st level: one 2-input NAND and six 3-input NAND

2nd level: one 7-input NAND

Simplification: use 3-level logic

1st level: $p_1 = a_1+b_1, g_1 = a_1b_1, p_0 = a_0+b_0, g_0 = a_0b_0,$

2nd and 3rd levels: $c_2 = g_1 + p_1g_0 + p_1p_0c_0$

Total gates: three 2-input AND, one 3-input AND
two 2-input OR, one 3-input OR



Carry Look Ahead (CLA) Adder

$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 c_1 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 c_2 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

$$c_4 = g_3 + p_3 c_3 = \underline{g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0} + \underline{p_3 p_2 p_1 p_0 c_0}$$

G_{30} P_{30}

$$g_i = a_i b_i \quad p_i = a_i + b_i$$

 



Carry Look Ahead (CLA) Adder

$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 c_1 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 c_2 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$


$$c_4 = g_3 + p_3 c_3 = \underline{g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0} + \underline{p_3 p_2 p_1 p_0 c_0}$$

G_{30} P_{30}


$$g_i = a_i b_i \quad p_i = a_i + b_i$$

 

CLA Adder Delay

 

 - Step 1: compute g_i and p_i signals for each single bit in parallel
- Step 2: compute G and P for 4-bit blocks
- Step 3: C_0 propagates through each 4-bit CLA block
- Step 4: compute sum, $s_i = p_i \oplus c_i$
- **Longest path: a_0 to s_{15}**




CLA Adder Delay

- Delay of an N -bit carry-lookahead adder with k -bit blocks:

$$t_{CLA} = t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA}$$

where

 - t_{pg} : delay of the column generate and propagate gates
- t_{pg_block} : delay of the block generate and propagate gates
- t_{AND_OR} : delay from C_{in} to C_{out} of the final AND/OR gate in the k -bit CLA block
- An N -bit carry-lookahead adder is generally much faster than a ripple-carry adder for $N > 16$



Subtractor

A subtracter inputs a two-bit number ($x_1; x_0$), a subtrahend ($y_1; y_0$) and a borrow-in bit b_0 , and outputs the difference ($d_1; d_0$) and a borrow-out bit b_2 . Write the boolean expression of borrow-out bit b_2 as a function of variables $x_1; x_0; y_1; y_0; b_0$.

Full subtracter
truth table

x_i	y_i	b_i	d_i	b_{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$d_i = x_i \oplus y_i \oplus b_i$$

$$b_{i+1} = x_i' y_i + x_i' b_i + y_i b_i$$

Therefore we have:

$$b_1 = x_0' y_0 + (x_0' + y_0) b_0$$

$$b_2 = x_1' y_1 + (x_1' + y_1) b_1$$

$$= x_1' y_1 + (x_1' + y_1) x_0' y_0 + (x_1' + y_1)(x_0' + y_0) b_0$$

Subtractor




Use two full adders and a minimal number of AND, OR, NOT gates to implement a look-ahead subtracter. Draw the schematic diagram.

The whole circuit is composed of 3 parts:

Step1: generate g_1 , g_0 and p_1 , p_0 in parallel.

$$g_i = x_i' y_i \quad p_i = x_i' + y_i$$

Step2: generate b_1 and b_2 in parallel.

 




$$b_1 = g_0 + p_0 b_0$$


$$b_2 = g_1 + p_1 g_0 + p_1 p_0 b_0$$

Step3: generate d_0 and d_1 using full adders.

$$d_0 = x_0 \oplus y_0 \oplus b_0$$

$$d_1 = x_1 \oplus y_1 \oplus b_1$$

   

 

Sequential Adder

A sequential adder inputs a_i ; b_i , the i^{th} bit of two binary numbers in each clock cycle for $i = 0$ to $n-1$ and outputs the sum s_i . Implement the adder with a JK flip-flop, and a minimal AND-OR-NOT network (if the network is needed). Draw the schematic diagram.

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$s_i = a_i' b_i' c_i + a_i' b_i c_i' + a_i b_i' c_i' + a_i b_i c_i$$

Where is c_i ?

Stored in the JK flip flop

Full adder truth table:

a_i	b_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

FSM state table:

a_i	b_i	CS	NS	s_i	J	K
0	0	0	0	0	0	X
0	0	1	0	1	X	1
0	1	0	0	1	0	X
0	1	1	1	0	X	0
1	0	0	0	1	0	X
1	0	1	1	0	X	0
1	1	0	1	0	1	X
1	1	1	1	1	X	0

$$J = a_i b_i$$

$$K = a_i' b_i'$$




6.5. Counter

Counters: Given **modulo-16 counters**, draw the logic diagram to show the following designs

- 6.5.1 Design a module-200 counter with a repeated output

Count through 0 to 199
 $(199)_{10} = (11000111)_2$

Reset the counter after it counts to 199

 




6.5. Counter

 - 6.5.2 Design a counter with a repeated output sequence **15, 0, 1, 2, 8, 9, 10, 6, 7**, with a **modulo-16 counter** and a minimal combinational network

9-cycle sequence → count from 0 to 8 and then reset

Need to map the counter output to the number sequence



Mapping logic

Q	O
0	0
1	1
2	2
3	8
4	9
5	10
6	6
7	7
8	15

6.5.2 Counter (Continued)



Mapping logic

Q	O
0	0
1	1
2	2
3	8
4	9
5	10
6	6
7	7
8	15

Truth table

Q3	Q2	Q1	Q0	O3	O2	O1	O0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	1	0	0	0
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	0
0	1	1	0	0	1	1	0
0	1	1	1	0	1	1	1
1	0	0	0	1	1	1	1

Kmap for O0

Q3Q2		00	01	11	10
Q1Q0		00	01	X	1
0	1	0	1	X	1
1	0	1	0	X	X
0	1	0	1	X	X
0	0	0	0	X	X

$$O_0 = Q_2 Q_1' Q_0' + Q_3 + Q_2' Q_1' Q_0 + Q_2 Q_1 Q_0$$

Kmap for O3

Q3Q2		00	01	11	10
Q1Q0		00	01	X	1
0	1	0	1	X	1
0	1	0	1	X	X
1	0	1	0	X	X
0	0	0	0	X	X

$$O_3 = Q_2 Q_1' + Q_3 + Q_2' Q_1 Q_0$$

Kmap for O2

Q3Q2		00	01	11	10
Q1Q0		00	01	X	1
0	0	0	0	X	1
0	0	0	0	X	X
0	1	0	1	X	X
0	1	0	1	X	X

$$O_2 = Q_2 Q_1 + Q_3$$

Kmap for O1

Q3Q2		00	01	11	10
Q1Q0		00	01	X	1
0	0	0	0	X	1
0	1	0	1	X	X
0	1	0	1	X	X
1	1	1	1	X	X

$$O_1 = Q_2 Q_0 + Q_3 + Q_1 Q_0'$$




6.6 Counter

- Design a counter with a repeated output sequence 0, 1, 2, 4, 5, 6, 3, with a modulo-8 counter and a minimal AND-OR-NOT network

7-cycle sequence → count from 0 to 6 and then reset

 Need to map the counter output to the number sequence



Mapping logic

Q	O
0	0
1	1
2	2
3	4
4	5
5	6
6	3




6.7 System Design

- *Alg(X, Y, Z, start, U, done);*
- *Input X[7 : 0], Y [7 : 0], Z[7 : 0], start;*
- *Output U[7 : 0], done;*
- Local-object A[7 : 0], B[7 : 0], C[7 : 0];
- S1: If start' goto S1;
- S2: done <= 0 || A <= X || B <= Y || C <= Z;
- S3: A <= Add(A;B);
- S4: If B'[7] goto S3 || B <= Inc(B);
- S5: If C'[7] goto S3 || C <= Inc(C);
- S6: U <= A || done <= 1 || goto S1;
- End Alg



6.7 System Architecture

 

The controller

- Reads **B[7]** and **C[7]** to determine the destination of “goto”
- Sends control signals (**Ct**) to datapath to perform the appropriate operations

6.7 Operations and Its Control Signals




	operation	control
$A \leq X$	$A \leftarrow \text{Load}(X)$	Ct_0
$B \leq Y$	$B \leftarrow \text{Load}(Y)$	Ct_1
$C \leq Z$	$C \leftarrow \text{Load}(Z)$	Ct_2
$A \leq A+B$	$A \leftarrow \text{Add}(A, B)$	Ct_3
$B \leq B+1$	$B \leftarrow \text{INC}(B)$	Ct_4
$C \leq C+1$	$C \leftarrow \text{INC}(C)$	Ct_5
$U \leq A$	Wires	

Hardware components needed:
One adder, two counters, a register




6.7 Datapath

 




6.7 FSM

- S1: If start' goto S1;
- S2: done <= 0 || A <= X || B <= Y || C <= Z;
- S3: A <= Add(A;B);
- S4: If B'[7] goto S3 || B <= Inc(B);
- S5: If C'[7] goto S3 || C <= Inc(C);
- S6: U <= A || done <= 1 || goto S1;

 



6.7 Controller Design

 

	Ct_0	Ct_1	Ct_2	Ct_3	Ct_4	Ct_5	done
state0	0	0	0	0	0	0	0
state1	1	1	1	0	0	0	0
state2	0	0	0	1	0	0	0
state3	0	0	0	0	1	0	0
state4	0	0	0	0	0	0	0
state5	0	0	0	0	0	1	0
state6	0	0	0	0	0	0	1