

CSE140 Discussion

Mingjing Chen

5/4

3.4 Sequential circuit check


S	R	Q	Q'
0	0	Q_{prev}	Q'_{prev}
0	1	0	1
1	0	1	0
1	1	1	1

Retain previous state

reset


set

invalid

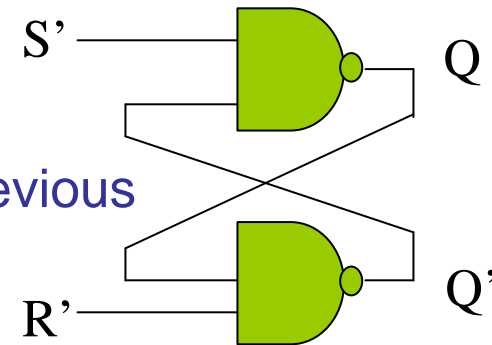


Still an SR latch

3.7 Flip-flop conversion: D → JK


 


J	K	Q	Q'
0	0	Q_{prev}	Q'_{prev}
0	1	0	1
1	0	1	0
1	1	Q'_{prev}	Q_{prev}

 

D	Q	Q'
0	0	1
1	1	0

 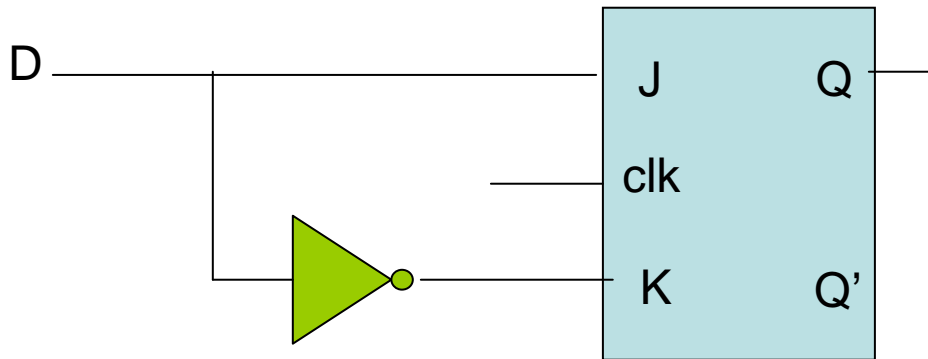3.7 Flip-flop conversion: JK \rightarrow D&T



Question:

D \rightarrow T

T \rightarrow D

Sequential circuit design flow

Step 1:

Circuit specification → FSM

Step 1:

FSM → Next state table. The table should show the present states, inputs, next states and outputs.

Step 2:

State encoding. If you have n states, your binary codes will have at least $\lceil \log_2 n \rceil$ digits, and your circuit will have at least $\lceil \log_2 n \rceil$ flip-flops.

Step 3:

Select flip-flop and create flip-flop excitation table. For each flip-flop and each row of your state table, find the flip-flop input values that generate the correct next state.

Step 4:

Find simplified equations for the flip-flop inputs and the outputs. You can use Kmap to derive each equation

Step 5:

Build the circuit!

3.26 FSM design

Specification:

Input: A, B

Outputs: Z

$$Z_n = A_n A_{n-1}, \text{ if } B_n = 0$$

$$Z_n = A_n + A_{n-1}, \text{ if } B_n = 1$$

Is this FSM a Moore machine or Mealy machine?

Mealy machine, as the output depends on the input value

3.26 FSM design

Specification:

Input: A, B


Outputs: Z

$$Z_n = A_n A_{n-1}, \text{ if } B_n = 0$$

$$Z_n = A_n + A_{n-1}, \text{ if } B_n = 1$$


Draw the FSM diagram

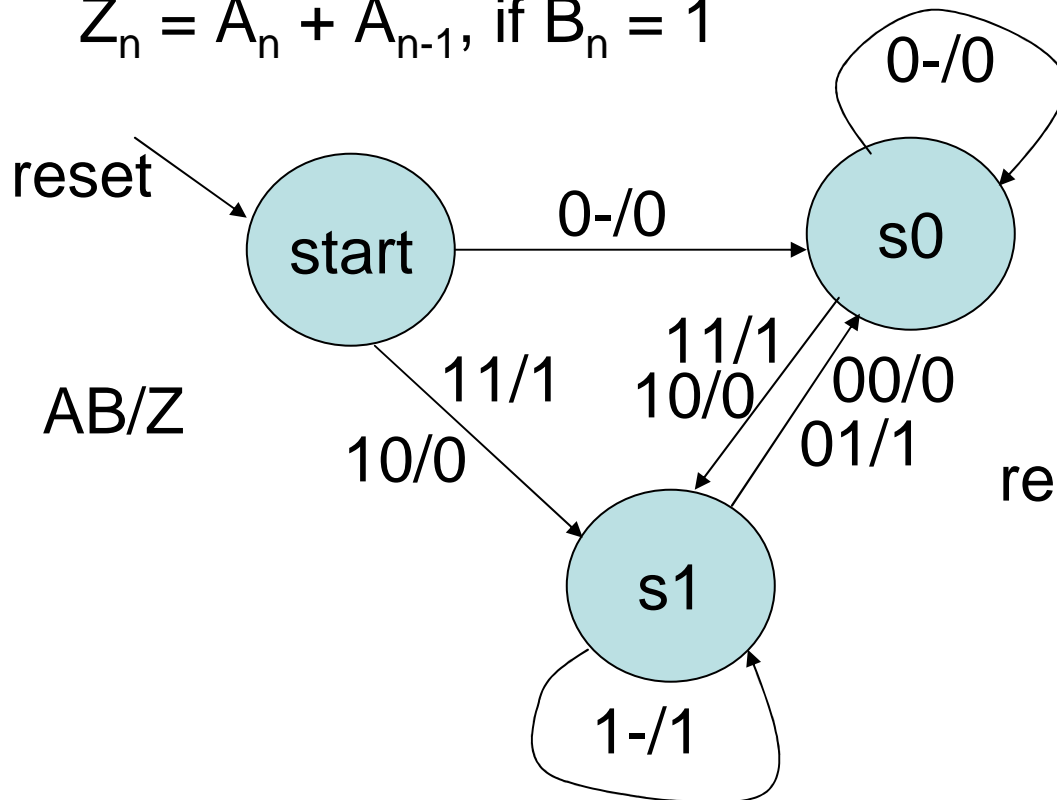Idea: need two states for memorizing A_{n-1}



Can it be optimized?

 No difference between Start & S0. They can be merged!



3.26 FSM design

Specification:


Input: A, B

Outputs: Z

$$Z_n = A_n A_{n-1}, \text{ if } B_n = 0$$

$$Z_n = A_n + A_{n-1}, \text{ if } B_n = 1$$

State encoding

 

A	B	Current state	Next state
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Next state equation:

$$Q_{\text{next}} = A$$

3.26 FSM design

Specification:

Input: A, B


Outputs: Z

$$Z_n = A_n A_{n-1}, \text{ if } B_n = 0$$

$$Z_n = A_n + A_{n-1}, \text{ if } B_n = 1$$

A	B	Current state	output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

State encoding

 

		AB			
		00	01	11	10
Q _{current}	0	0	0	1	0
	1	0	1	1	1

Output equation:

$$Z = AB + BQ + AQ$$

3.26 FSM design

Specification:

Input: A, B

Outputs: Z

$$Z_n = A_n A_{n-1}, \text{ if } B_n = 0$$

$$Z_n = A_n + A_{n-1}, \text{ if } B_n = 1$$


Next state equation:

$$Q_{\text{next}} = A$$

Output equation:

$$Z = AB + BQ + AQ$$

Use D flip-flop

 

Question:

How to design the circuit using JK flip-flop?