

## Sample Midterm #1 Solution

1. Prove using Boolean algebra that  $a'c' + ab + ac + a'b' = a'c' + ab + b'c$ . Write the particular law you are using in each step.

$$\begin{aligned}
 \text{Proof: } & a'c' + ab + ac + a'b' \\
 &= a'c' + ab + (ac + a'b') && \text{associativity} \\
 &= a'c' + ab + (ac + a'b' + b'c) && \text{consensus} \\
 &= a'c' + ab + ac + a'b' + b'c + b'c && \text{idempotency} \\
 &= (a'c' + b'c + a'b') + (ab + b'c + ac) && \text{commutativity+ associativity} \\
 &= (a'c' + b'c) + (ab + b'c) && \text{consensus} \\
 &= a'c + ab + b'c && \text{idempotency}
 \end{aligned}$$

2. Prove using Boolean algebra that  $(a + c)(a' + c')(b' + c + d')(a + b' + d') = (a + c)(a' + c')(b' + d')$ . Write the particular law you are using in each step.

$$\begin{aligned}
 \text{Proof: } & (a + c)(a' + c')(b' + c + d')(a + b' + d') \\
 &= (a + c)(a' + c')((ac) + (b' + d')) && \text{distributivity} \\
 &= (a + c)(a' + c')ac + (a + c)(a' + c')(b' + d') && \text{distributivity} \\
 &= (a + c)(a'ac + c'ac) + (a + c)(a' + c')(b' + d') && \text{distributivity} \\
 &= (a + c)(0 + 0) + (a + c)(a' + c')(b' + d') && \text{complement} \\
 &= 0 + (a + c)(a' + c')(b' + d') && \text{nullity} \\
 &= (a + c)(a' + c')(b' + d') && \text{identity}
 \end{aligned}$$

3. Use Karnaugh map to simplify function  $f(a, b, c, d) = \sum m(0,1, 2, 3, 4, 5, 7,8,12) + \sum d(10,11)$ . List **all possible** minimal two-level **sum of products** expressions.

Show the switching functions. No need for the diagram.

		ab			
		00	01	11	10
cd	00	1	1	1	1
	01	1	1		
	11	1	1		x
	10	1			x

$$\begin{aligned}
 & F = a'd + a'b' + c'd' \\
 \text{or } & F = a'd + b'c + c'd' \\
 \text{or } & F = a'd + c'd' + b'd'
 \end{aligned}$$

4. Use Karnaugh map to simplify function  $f(a, b, c, d) = \sum m(0,1, 2, 3, 4, 5, 7,8,12) + \sum d(10,11)$ . List **all possible** minimal two-level **product of sums** expressions. Show the switching functions. No need for the diagram.

	ab			
cd	00	01	11	10
00	1	1	1	1
01	1	1		
11	1	1		x
10	1			x

$$F = (a' + d') (a' + c') (b' + c' + d)$$

5. Universal Set of Gates: Check if the set in the following list is universal and explain your decision. Assuming constants 0 and 1 are available as inputs.


Solution: We know {AND, OR, NOT} is universal. If we can construct these three gates using the ones from the gate set we are checking, then the gate set under checking is also universal.

i. {AND, NOT}

AND, NOT already exist, only need to construct OR




ii. {NAND}

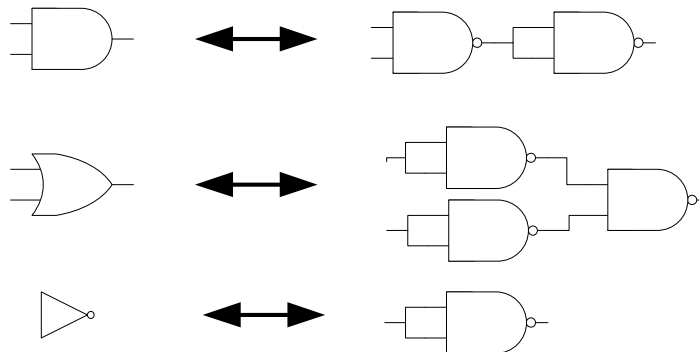

iii. {XOR, NOT}

Not universal, because AND or OR can not be constructed using XOR & NOT

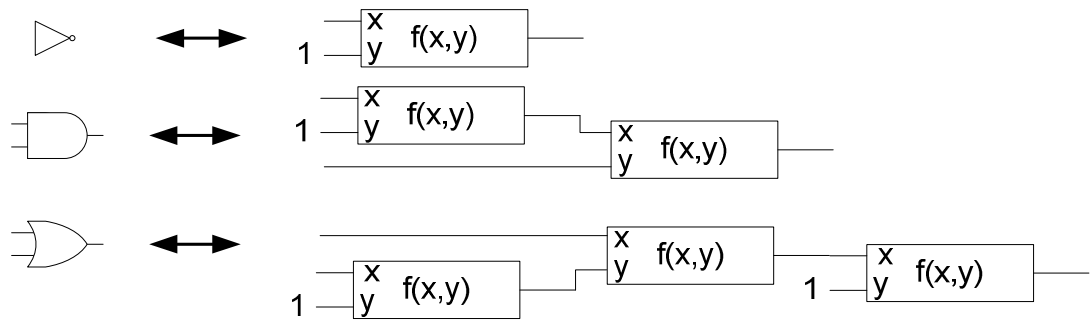iv.  $\{f(x,y)\}$ , where  $f(x,y) = x'y$



v. Universal, because  $(x+y)z'$  can easily reduce to  $xz'$  or  $yz'$  by connecting 0 to  $y$  or  $x$ . We have already proven that  $xz'$  is a universal gate in iv.

vi. Universal, because  $g(x,y) = x'y' = (x+y)'$ . The NOR gate is a universal gate.